

Capacitance

Mark Scheme 1

| | |
|------------|-----------------------|
| Level | International A Level |
| Subject | Physics |
| Exam Board | CIE |
| Topic | Capacitance |
| Sub Topic | |
| Paper Type | Theory |
| Booklet | Mark Scheme 1 |

Time Allowed: 83 minutes

Score: /69

Percentage: /100

CHEMISTRY ONLINE

| | | | | | | |
|------|-------|-----|-------|-------|-----|------|
| A* | A | B | C | D | E | U |
| >85% | 77.5% | 70% | 62.5% | 57.5% | 45% | <45% |


- 1 (a) for the two capacitors in parallel, capacitance = $96 \mu\text{F}$
for complete arrangement, $1/C_T = 1/96 + 1/48$
 $C_T = 32 \mu\text{F}$ C
A1 [2]
- (b) p.d. across parallel combination is one half p.d. across single capacitor
total p.d. = 9V C1
A [2]
- 2 (a) (i) energy = EQ C1
 $= 9.0 \times 22 \times 10^{-3}$
 $= 0.20 \text{ J}$ A1 [2]
- (ii) 1. $C = Q/V$
 $V = (22 \times 10^{-3})/(4700 \times 10^{-6})$ C1
 $= 4.7 \text{ V}$ A1 [2]
2. either $E = \frac{1}{2}CV^2$ C1
 $= \frac{1}{2} \times 4700 \times 10^{-6} \times 4.7^2$
 $= 5.1 \times 10^{-2} \text{ J}$ A1 [2]
- or $E = \frac{1}{2}QV$ (C1)
 $= \frac{1}{2} \times 22 \times 10^{-3} \times 4.7$
 $= 5.1 \times 10^{-2} \text{ J}$ (A1)
- or $E = \frac{1}{2}Q^2/C$ (C1)
 $= \frac{1}{2} \times (22 \times 10^{-3})^2 / 4700 \times 10^{-6}$
 $= 5.1 \times 10^{-2} \text{ J}$ (A1)
- (b) energy lost (as thermal energy) in resistance/wires/battery/resistor B1 [1]
(award only if answer in (a)(i) > answer in (a)(ii)2)

3 (a) e.g. store energy (do not allow 'store charge')
 in smoothing circuits
 blocking d.c.
 in oscillators
any sensible suggestions, one each, max. 2 B2 [2]

(b) (potential across each capacitor is the same and $Q = CV$ B1 [1]


(ii) total charge $Q = Q_1 + Q_2 + Q_3$ M1
 $CV = C_1V + C_2V + C_3V$ M1
 (allow $Q = CV$ here or in (i))
 so $C = C_1 + C_2 + C_3$ A0 [2]

(c)

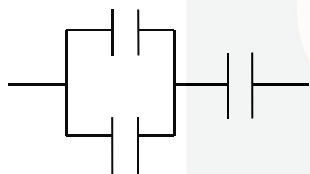

A1 [1]

(ii)

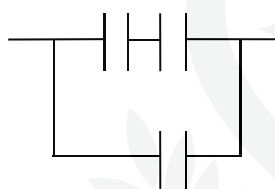

A1 [1]

CHEMISTRY ONLINE
 — TUITION —

- 4 (a) (i) ratio of charge and potential (difference)/voltage
(*ratio must be clear*) 81 [1]
- (ii) capacitor has equal magnitudes of (+)ve and (-)ve charge 81
total charge on capacitor is zero (so does not store charge) 81
(+)ve and (-)ve charges to be separated M1
work done to achieve this so stores energy A1 [4]
- (b) (i) capacitance of Y and Z together is 24 μF C1
 $1/C = 1/24 + 1/12$
 $C = 8.0 \mu\text{F}$ (*allow 1 s.f.*) A1 [2]
- (ii) some discussion as to why all charge of one sign on one plate of X 81
 $Q = (CV) = 8.0 \times 10^{-6} \times 9.0$ M1
 $= 72 \mu\text{C}$ AO [2]
- (iii) 1. $V = (72 \times 10^{-6}) / (12 \times 10^{-6})$
 $= 6.0\text{V}$ (*allow 1 s.f.*) (*allow 72/12*) A1 [1]
2. either $Q = 12 \times 10^{-6} \times 3.0$ or charge is shared between Y and Z C1
charge = $36 \mu\text{C}$ A1 [2]
Must have correct voltage in (iii) 1 if just quote of $36 \mu\text{C}$ in (iii) 2.
- 5 (a) e.g. storing energy
separating charge
blocking d.c.
producing electrical oscillations
tuning circuits
smoothing
preventing sparks
timing circuits
(*any two sensible suggestions, 1 each, max 2*) B2 [2]
- (b) (i) $-Q$ (induced) on opposite plate of C_1 B1
by charge conservation, charges are $-Q, +Q, -Q, +Q, -Q$ B1 [2]
- (ii) total p.d. $V = V_1 + V_2 + V_3$ B1
 $Q/C = Q/C_1 + Q/C_2 + Q/C_3$ B1
 $1/C = 1/C_1 + 1/C_2 + 1/C_3$ A0 [2]
- (c) (i) energy = $\frac{1}{2}CV^2$ or energy = $\frac{1}{2} QV$ and $C = Q/V$ C1
 $= \frac{1}{2} \times 12 \times 10^{-6} \times 9.0^2$
 $= 4.9 \times 10^{-4} \text{ J}$ A1 [2]
- (ii) energy dissipated in (resistance of) wire/as a spark B1 [1]

6 (a) charges on plates are equal and opposite
so no resultant charge
energy stored because there is charge separation

M1
A1
81 [3]

(b) (i) capacitance = Q/V
: $(18 \times 10^{-3}) / 10$
= $1800 \mu\text{F}$

C1
A1 [2]

(ii) use of area under graph or energy = $\frac{1}{2}CV^2$
energy = $2.5 \times 15.7 \times 10^{-3}$ or energy = $\frac{1}{2} \times 1800 \times 10^{-6} \times (1a^2 - 7.5^2)$
= 39mJ

C1
A1 [2]

(c) combined capacitance of Y & Z = $20 \mu\text{F}$ or total capacitance = $6.67 \mu\text{F}$
p.d. across capacitor X = 8V or p.d. across combination = 12V
charge = $10 \times 10^{-6} \times 8$ or $6.67 \times 10^{-6} \times 12$
= $80\mu\text{C}$

C1
C1
A1 [3]

7 (a) charge / potential (difference) (*ratio must be clear*)

B1 [1]

(b) (i) $V = Q / 4\pi\epsilon_0 r$

B1 [1]

(ii) $C = Q / V = 4\pi\epsilon_0 r$ and $4\pi\epsilon_0$ is constant
so $C \propto r$

M1
A0 [1]

(c) (i) $r = C / 4\pi\epsilon_0$
 $r = (6.8 \times 10^{-12}) / (4\pi \times 8.85 \times 10^{-12})$
= $6.1 \times 10^{-2}\text{m}$

C1
C
A [3]

(ii) $Q = CV = 6.8 \times 10^{-12} \times 220$
= $1.5 \times 10^{-9}\text{C}$

A1 [1]

(d) (i) $V = Q/C = (1.5 \times 10^{-9}) / (18 \times 10^{-12})$
= 83V

A1 [1]

(ii) either energy = $\frac{1}{2}CV^2$
 $\Delta E = \frac{1}{2} \times 6.8 \times 10^{-12} \times 220^2 - \frac{1}{2} \times 18 \times 10^{-12} \times 83^2$
= $1.65 \times 10^{-7} - 6.2 \times 10^{-8}$
= $1.03 \times 10^{-7}\text{J}$
or energy = $\frac{1}{2}QV$
 $\Delta E = \frac{1}{2} \times 1.5 \times 10^{-9} \times 220 - \frac{1}{2} \times 1.5 \times 10^{-9} \times 83$
= $1.03 \times 10^{-7}\text{J}$

C1
C1
A [3]
(C1)
(C1)
(A1)

- 8 (a) (i) work done moving unit positive charge from infinity to the point M1
A1 [2]
- (ii) charge / potential (difference) (ratio must be clear) B [1]
- (b) (i) capacitance = $(2.7 \times 10^{-6}) / (150 \times 10^3)$ C
(allow any appropriate values)
capacitance = 1.8×10^{-11} (allow 1.8 ± 0.05) A1 [2]
- (ii) either energy = $\frac{1}{2}CV^2$ or energy = $\frac{1}{2}QV$ and $Q = CV$ C1
energy = $\frac{1}{2} \times 1.8 \times 10^{-11} \times (150 \times 10^3)^2$ or $\frac{1}{2} \times 2.7 \times 10^{-6} \times 150 \times 10^3$
= 0.20 J A1 [2]
- (c) either since energy $\propto V^2$, capacitor has $(\frac{1}{2})^2$ of its energy left C1
or full formula treatment A1 [2]
energy lost = 0.15 J