

Capacitance

Mark Scheme 2

Level	International A Level
Subject	Physics
Exam Board	CIE
Topic	Capacitance
Sub Topic	
Paper Type	Theory
Booklet	Mark Scheme 2

Time Allowed: 88 minutes

Score: /73

Percentage: /100

CHEMISTRY ONLINE

A*	A	B	C	D	E	U
>85%	77.5%	70%	62.5%	57.5%	45%	<45%

- 1 (a) e.g. 'storage of charge' / storage of energy
blocking of direct current
producing of electrical oscillations
smoothing
(any two, 1 mark each) B2 [2]
- (b) (i) capacitance of parallel combination = $60 \mu\text{F}$ C1
total capacitance = $20 \mu\text{F}$ A1 [2]
- (ii) p.d. across parallel combination = $\frac{1}{2} \times$ p.d. across single capacitor C1
maximum is 9V A1 [2]
- (c) either energy = $\frac{1}{2}CV^2$ or energy = $\frac{1}{2}QV$ and $Q = CV$ C1
energy = $\frac{1}{2} \times 4700 \times 10^{-6} \times (18^2 - 12^2)$ C
= 0.42 J A1 [3]
- 2 (a) charge / potential(ratio must be clear) B1 [1]
- (b) potential (at surface of sphere) = $Q / 4\pi\epsilon_0 R$ M1
 $C = Q / V = 4\pi\epsilon_0 R$ A0 [1]
- (c) (i) $C = 4\pi \times 8.85 \times 10^{-12} \times 0.63$ C1
= 7.0×10^{-11} A1
farad / F B1 [3]
- (ii) energy = $\frac{1}{2}CV^2$ C1
 $0.25 \times \frac{1}{2}C \times (1.2 \times 10^6)^2 = \frac{1}{2}CV^2$ C1
 $V = 6.0 \times 10^5 \text{ V}$ A1 [3]
(use of 0.75 rather than 0.25, allow max 2 marks)

[Total: 8]

3 (a) (i) ratio of charge (on body) and its potential
(do not allow reference to plates of a capacitor) B1 [1]

(ii) (potential at surface of sphere $\Rightarrow V = Q / 4\pi\epsilon_0 r$ M1
 $C = Q / V = 4\pi\epsilon_0 r$ A0 [1]

(b) (i) $C = 4 \times \pi \times 8.85 \times 10^{-12} \times 0.36$
 $= 4.0 \times 10^{-11} \text{ F (allow 1 s.f.)}$ A1 [1]

(ii) $Q = CV$
 $= 4.0 \times 10^{-11} \times 7.0 \times 10^5$
 $= 2.8 \times 10^{-5} \text{ C}$ A1 [1]

(c) plastic is an insulator / not a conductor / has no free electrons B1
charges do not move (on an insulator) B1
either so no single value for the potential
or charge cannot be considered to be at centre B1 [3]

(d) either energy $= \frac{1}{2}CV^2$ or energy $= \frac{1}{2}QV$ and $C = Q/V$ C1
energy $= \frac{1}{2} \times 4 \times 10^{-11} \times \{(7.0 \times 10^5)^2 - (2.5 \times 10^5)^2\}$
 $= 8.6 \text{ J}$ A [3]

4 (a) at $t = 1.0 \text{ s}$, $V = 2.5 \text{ V}$ C1
energy $= \frac{1}{2}CV^2$ C1
 $0.13 = \frac{1}{2} \times C \times (8.0^2 - 2.5^2)$ M
 $C = 4500 \mu\text{F}$ A [3]

(b) use of two capacitors in series in all branches of combination M1
connected into correct parallel arrangement A1 [2]

- 5 (a) e.g. separate charges, store energy, smoothing circuit. etc. B1 [1]
(allow 'stores charge')
- (b) (i) charge = current \times time B1 [1]
- (ii) area is 21.2 cm^2 (allow $\pm 0.5 \text{ cm}^2$) C2
(allow 1 mark if outside $\pm 0.5 \text{ cm}^2$ but within $\pm 1.0 \text{ cm}^2$)
1.0 cm^2 represents $(0.125 \times 10^{-3} \times 1.25 =) 156 \mu\text{C}$ C1
charge = $3300 \mu\text{C}$ A1 [4]
- (iii) capacitance = Q/V C1
= $(3300 \times 10^{-6}) / 15$
= $220 \mu\text{F}$ A1 [2]
- (c) either energy = $\frac{1}{2}CV^2$ or energy = $\frac{1}{2}QV$ and $C = Q/V$ C1
 $\frac{1}{2} \times C \times 15^2 = 2 \times \frac{1}{2} \times C \times V^2$ C1
 $V = 10.6 \text{ V}$ A1 [3]
- 6 (a) (i) peak voltage = $6\sqrt{2}$ C1
peak voltage = 8.48 V A1 [2]
- (ii) zero because either no current in circuit (and $V = IR$)
or all p.d. across diode B1 [1]
- (b) waveform: half-wave rectification B1
peak height at about 4.25 cm B1
half-period spacing of 2.0 cm B1 [3]
(allow $\pm \frac{1}{4}$ square for height and half-period)
- (c) (i) capacitor shown in parallel with resistor B1 [1]
- (ii) either energy = $\frac{1}{2}CV^2$ or = $\frac{1}{2}QV$ and $Q = CV$ C1
= $\frac{1}{2} \times 180 \times 10^{-6} \times (6\sqrt{2})^2$ C1
= $6.48 \times 10^{-3} \text{ J}$ A1 [3]
- (iii) either fraction = 0.43^2 or final energy = 1.2 mJ C1
fraction = 0.18 A1 [2]

- 7 (a) Q/V , with symbols explained [do not allow in terms of units] **B1** [1]
- (b) (on a capacitor, there is charge separation/there are + and - charges **M1**
either to separate charges, work must be done
or energy released when charges 'come together' **A1** [2]
- (ii) either energy = $\frac{1}{2}CV^2$ or energy = $\frac{1}{2}QV$ and $C = Q/V$ **C1**
change = $\frac{1}{2} \times 1200 \times 10^{-6} (50^2 - 15^2)$ **C1**
change = 1.4 J (1.37) **A1** [3]
[allow 2 marks for $\frac{1}{2}C(\Delta V)^2$, giving energy = 0.74 J]
- 8 (a) two capacitors in series
or any circuit such that $V = 25$ V across any C **B1**
in parallel with second series pair or any correct combination **B1** [2]
- (b) two capacitors in series in parallel with a single capacitor
or other correct combination **B2** [2]
{leads not shown, then -1 overall}
- 9 (a) single diode.....**M1**
in series with R OR in series with a.c. supply **A1** [2]
- (b) (i)1 5.4 V (allow ± 0.1 V)..... **A1**
- (i)2 $V = iR$
 $I = 5.4/1.5 \times 10^3$ **C1**
 $= 3.6 \times 10^{-3}$ A **A1**
- (i)3 time = 0.027 s **A1** [4]
- (ii) $Q = it$
 $= 3.6 \times 10^{-3} \times 0.027$ **C1**
 $= 9.72 \times 10^{-5}$ C **A1**
- (ii) $C = \Delta Q/\Delta V$ (allow $C = Q/V$ for this mark) **C1**
 $= (9.72 \times 10^{-5})/1.2$
 $= 8.1 \times 10^{-5}$ F **A1** [4]
- (c) line: reasonable shape with less ripple **B1** [1]