Resistance & Resistivity Question paper 2

Level	International A Level		
Subject	Physics		
Exam Board	CIE		
Торіс	Current of Electricity		
Sub Topic	Resistance & Resistivity		
Paper Type	Theory		
Booklet	Question paper 2		

Time Allowed:	80 minutes		
Score:	/66		
Percentage:	/100		

CHEMISTRY ONLINE

A*	A	В	С	D	E	U
>85%	'77.5%	70%	62.5%	57.5%	45%	<45%

1 An electric heater has a constant resistance and is rated as 1.20 kW, 230 V.

The heater is connected to a 230V supply by means of a cable that is 9.20m long, as illustrated in Fig. 8.1.



The two copper wires that make up the cable each have a circular cross-section of diameter 0.900 mm. The resistivity of copper is $1.70 \times 10^{-8} \Omega m$.

- (a) Show that
 - (i) the resistance of the heater is 44.1Ω ,

[2]

(ii) the total resistance of the cable is 0.492Ω .

(b) The current in the cable and heater is switched on. Determine, to three significant figures, the power dissipated in the heater.

power = W [3]

(c) Suggest two disadvantages of connecting the heater to the 230V supply using a cable consisting of two thinner copper wires.

CHEMISTRY ONLINE — TUITION —

2 (a) Two resistors, each of resistance *R*, are connected first in series and then in parallel.

Show that the ratio

combined resistance of resistors connected in series combined resistance of resistors connected in parallel

is equal to 4.



[1]

(b) The variation with potential difference V of the current I in a lamp is shown in Fig. 6.1.



Calculate the resistance of the lamp for a potential difference across the lamp of 1.5V.

resistance = Ω [2]

(c) Two lamps, each having the I-V characteristic shown in Fig. 6.1, are connected first in series and then in parallel with a battery of e.m.f. 3.0V and negligible internal resistance.

Complete the table of Fig. 6.2 for the lamps connected to the battery.

	p.d. across each lamp/V	resistance of each lamp/ Ω	combined resistance of lamps/ Ω	
lamps connected in series				
lamps connected in parallel				

Fig. 6.2

[4]

(d) (i) Use data from the completed Fig. 6.2 to calculate the ratio

combined resistance of lamps connected in series combined resistance of lamps connected in parallel

ratio =[1]

(ii) The ratios in (a) and (d)(i) are not equal.

By reference to Fig. 6.1, state and explain qualitatively the change in the resistance of a lamp as the potential difference is changed.

Dr. Asher Rana www.chemistryonlinetuition.com asherrana@chemistryonlinetuition.com [3]

3 An electric shower unit is to be fitted in a house. The shower is rated as 10.5 kW, 230 V. The shower unit is connected to the 230 V mains supply by a cable of length 16 m, as shown in Fig. 6.1.



(a) Show that, for normal operation of the shower unit, the current is approximately 46 A.

[2]

(b) The resistance of the two wires in the cable causes the potential difference across the shower unit to be reduced. The potential difference across the shower unit must not be less than 225V.

The wires in the cable are made of copper of resistivity 1.8 $10^{-8}\Omega$ m. Assuming that the current in the wires is 46 A, calculate

(i) the maximum resistance of the cable,

(ii) the minimum area of cross-section of each wire in the cable.



- (c) Connecting the shower unit to the mains supply by means of a cable having wires with too small a cross-sectional area would significantly reduce the power output of the shower unit.
 - (i) Assuming that the shower is operating at 210V, rather than 230V, and that its resistance is unchanged, determine the ratio

power dissipated by shower unit at 210V power dissipated by shower unit at 230V



(ii) Suggest and explain one further disadvantage of using wires of small cross-sectional area in the cable.

- **4** A straight wire of unstretched length *L* has an electrical resistance *R*. When it is stretched by a force *F*, the wire extends by an amount ΔL and the resistance increases by ΔR . The area of cross-section *A* of the wire may be assumed to remain constant.
 - (a) (i) State the relation between *R*, *L*, *A* and the resistivity ρ of the material of the wire.

.....[1] (ii) Show that the fractional change in resistance $\frac{\Delta r}{R}$ ΔR ain in the wire.

(b) A steel wire has area of cross-section 1.20×10^{-7} m² and a resistance of 4.17Ω .

The Young modulus of steel is 2.10×10^{11} Pa.

The tension in the wire is increased from zero to 72.0 N. The wire obeys Hooke's law at these values of tension.

Determine the strain in the wire and hence its change in resistance. Express your answer to an appropriate number of significant figures.

change = $\dots \Omega$ [5]

[2]

5 Fig. 6.1 shows the variation with applied potential difference *V* of the current *I* in an electrical component C.



Fig. 6.1

(a) (i) State, with a reason, whether the resistance of component C increases or decreases with increasing potential difference.

(ii) Determine the resistance of component C at a potential difference of 4.0 V.

resistance = Ω [2]

(b) Component C is connected in parallel with a resistor R of resistance 1500Ω and a battery of e.m.f. *E* and negligible internal resistance, as shown in Fig. 6.2.



- (i) On Fig. 6.1, draw a line to show the variation with potential difference *V* of the current *I* in resistor R. [2]
- (ii) Hence, or otherwise, use Fig. 6.1 to determine the current in the battery for an e.m.f. of 2.0 V.

current = A [2]

(c) The resistor R of resistance 1500Ω and the component C are now connected in series across a supply of e.m.f. 7.0 V and negligible internal resistance.

Using information from Fig. 6.1, state and explain which component, R or C, will dissipate thermal energy at a greater rate.

[3]

- **6** A household electric lamp is rated as 240 V, 60 W. The filament of the lamp is made from tungsten and is a wire of constant radius 6.0×10^{-6} m. The resistivity of tungsten at the normal operating temperature of the lamp is $7.9 \times 10^{-7} \Omega$ m.
 - (a) For the lamp at its normal operating temperature,
 - (i) calculate the current in the lamp,

current =A (ii) show that the resistance of the filament is 960Ω . [3] (b) Calculate the length of the filament. length = m [3] (c) Comment on your answer to (b).[1] 7 A filament lamp operates normally at a potential difference (p.d.) of 6.0 V. The variation with p.d. V of the current **I** in the lamp is shown in Fig. 5.1.



Fig.5.1

- (a) Use Fig. 5.1 to determine, for this lamp,
 - \ref{main} the resistance when it is operating at a p.d. of 6.0 V,



resistance = n

(ii) the change in resistance when the p.d. increases from 6.0 V to 8.0 V.





200Q

R is a fixed resistor of resistance 200 $\rm m$. The battery has e.m.f. E and negligible internal resistance.

- (i) On Fig. 5.1, draw a line to show the variation with p.d. **V** of the current **I** in the resistor **R**.
- (ii) Determine the e.m.f. of the battery for the lamp to operate normally.