Current, Potential Difference & Power

Mark Scheme 1

Level	International A Level
Subject	Physics
Exam Board	CIE
Торіс	Current of Electricity
Sub Topic	Current, Potential Difference & Power
Paper Type	Theory
Booklet	Mark Scheme 1

Time Allowe	d:	80 minutes	80 minutes				
Score:		/66					
Percentage:		/100					
A*	A	В	С	D	E	U	
>85%	'77.5%	70%	62.5%	57.5%	45%	<45%	

1	(a	e.m.f.: energy converted from chemical/other forms to electrical per unit charge p.d.: energy converted from electrical to other forms per unit char	B1 B1	[2]
	(b)	 (i) the p.d. across the lamp is <u>less than</u> 12V or there are lost volts/power/energy in the battery/internal resistance (ii) R = V²/P (or V = RI and P = VI) = 144/48 = 3.0 Ω 	B1 C A1	[1] [2]
		(iii) $I = E/(R_T + r)$ = 12/2.0 = 6.0 A	C A1	[2]
		(iv) power of each lamp = $I^2 R$ = $(3.0)^2 \times 3.0$ = 27 W	C1 A	[2]
	(c)	less resistance (in circuit)/more current more lost volts/less p.d. across battery	M1 A1	[2]

2	(a	p.d. = work (done) / charge OR energy transferred from (electrical to other forms) / (unit) charge	B1	[1]
	(b)	(i) $R = \rho l / A$ $\rho = 18 \times 10^{-9}$ $R = (18 \times 10^{-9} \times 75) / 2.5 \times 10^{-6} = 0.54 \Omega$	C1 C1 A1	[3]
		(ii) $V = IR$ $R = 38 + (2 \times 0.54)$ I = 240 / 39.08 = 6.1 (6.14) A	C1 C1 A1	[3]
		(iii) $P = I^2 R \text{ or } P = VI \text{ and } V = IR \text{ or } P = V^2 / R \text{ and } V = IR$ = $(6.14)^2 \times 2 \times 0.54$ = 41 (40.7) W	C1 C1 A1	[3]
	(c) C	area of wire is less (1/5) hence resistance greater (×5)) DR <i>R</i> is \propto 1/A therefore <i>R</i> is greater p.p.d. across wires greater so power loss in cables increas	A1	[2]

3	(a (i) chemical to electrical	B1	[1]
	(ii) electrical to thermal / heat or heat and light	B1	[1]
	(b) (i) $(P_{\rm B}=) EI \text{ or } I^2(R_1+R_2)$	А	[1]
	(ii) $(P_{\rm R} =) I^2 R_1$	A1	[1]
	(c) $R = \rho l / A$ or clear from the following equation	B1	
	ratio = $I^2 R_1 / I^2 R_2 = \frac{\rho l / \pi d^2}{\rho (2l) / \pi (2d)^2}$ or R_1 has 8× resistance of R_2	C1	
	= 8 or 8:1	A1	[3]
	(d) $P = V^2 / R$ or E^2 / R (<i>V</i> or <i>E</i> the same) hence ratio is 1/8 or 1:8 = 0.125 (allow ecf from (c))	C1 A1	[2]
4	(a charge = current × time	B1	[1]
	(b) (i) $P = V^2 / R$ = $(240)^2 / 18 = 3200 W$	C1 A	[2]
	(ii) $I = V / R = 240 / 18 = 13.3 \text{ A}$	А	[1]
	(iii) charge = $It = 13.3 \times 2.6 \times 10^6$ = 3.47 × 10 ⁷ C	C1 A1	[2]

(iv) number of electrons = $3.47 \times 10^7 / 1.6 \times 10^{-19} (= 2.17 \times 10^{26})$ C1 number of electrons per second = $2.17 \times 10^{26} / 2.6 \times 10^6 = 8.35 \times 10^{19}$ A1 [2]

5	(a)	p.d.	= <u>work done / energy transformed</u> (from electrical to other forms) charge	B1	[1]
	(b)	(i)	maximum 20 V	A1	[1]
		(ii)	minimum = (600 / 1000) × 20 = 12 V	C1 A1	[2]
	(c)	(i)	use of $1.2 k\Omega$ 1/1200 + 1/600 = 1/ <i>R</i> , <i>R</i> = 400 Ω	M1 A1	[2]
		(ii)	total parallel resistance (R_2 + LDR) is less than R_2 (minimum) p.d. is reduced	M1 A1	[2]
6	(a) (i)	$R = V^2 / P \text{ or } P = IV \text{ and } V = IR$		
	(1	, (,	$= (220)^2 / 2500$ = 19.4\Omega (allow 2 s.f.) A1	[2]	
		(ii)	$R = \rho l / A$ $l = [19.4 \times 2.0 \times 10^{-7}] / 1.1 \times 10^{-6}$ $= 3.53 \text{ m} (allow 2 \text{ s.f.})$ C1	[3]	
	(b) (i)	P = 625, 620 or 630 W A1	[1]	
		(ii)	R needs to be reduced C1 Either length ¼ of original length or area 4× greater		
			or diameter 2× greater A1	[2]	

7	(a)	total resistance = 20 (k Ω) current = 12 / 20 (mA) or potential divider formula	C1 C1	
		p.d. = [12 / 20] × 12 = 7.2 V	A1	[3]

- (b) parallel resistance = $3 (k\Omega)$ C1

 total resistance $8 + 3 = 11 (k\Omega)$ C1

 current = $12 / 11 \times 10^3 = 1.09 \times 10^{-3}$ or 1.1×10^{-3} A
 A1
 [3]
- (c) (i)LDR resistance decreases
total resistance (of circuit) is less hence current increasesM1
A1[2](ii)resistance across XY is less
less proportion of 12 V across XY hence p.d. is lessM1
A1[2]

