

Resistance & Resistivity

Mark Scheme 2

Level	International A Level
Subject	Physics
Exam Board	CIE
Topic	Current of Electricity
Sub Topic	Resistance & Resistivity
Paper Type	Theory
Booklet	Mark Scheme 2

Time Allowed: 80 minutes

Score: /66

Percentage: /100

CHEMISTRY ONLINE

A*	A	B	C	D	E	U
>85%	77.5%	70%	62.5%	57.5%	45%	<45%

- 1 (a) (i) either $P = V^2 / R$ o $I = 1200 / 230$ or 5.22 C1
 $R = 230^2 / 1200$ or $R = 230 / 5.22$ M1
 $= 44.1 \Omega$ = 44.1 Ω A0 [2]
- (ii) $R = \rho L / A$ C1
 $= (1.7 \times 10^{-8} \times 9.2 \times 2) / (\pi \times \{0.45 \times 10^{-3}\}^2)$ M
 $= 0.492 \Omega$ A0 [2]
- (b) current = 230 / 44.6 C1
power = $(230 / 44.6)^2 \times 44.1$ C1
= 1170 W A [3]
(allow full credit for solution based on potential divider)
- (c) e.g. less power dissipated in the heater / smaller p.d. across heater /
more power loss in cable / current lower B1
cable becomes heated / melts B1 [2]
(any two sensible suggestions, 1 each, max 2)

CHEMISTRY ONLINE
— TUITION —

- 2 (a) total resistance in series = $2R$ M1
 total resistance in parallel = $\frac{1}{2}R$ A0 [1]
 ratio is $2R / \frac{1}{2}R = 4$ (allow mark if clear numbers in the ratio)A0

- (b) at 1.5 V, current is 0.10 AC1
 resistance = $V/I = \frac{1.5}{0.1}$ A1 [2]
 = 15 Ω A1
 (use of tangent or any other current scores no marks)

(c)

	p.d. across each lamp / V	resistance of each lamp / Ω	combined resistance / Ω
series	1.5	15	30
parallel	3.0	20	10

- column 1A1
 columns 2 and 3: max 3 marks with -1 mark for each error or omissionA3 [4]

- (d) (ratio is 3(allow e.c.f.)A1 [1]
 (ii) resistance increases as potential difference increasesB1
 increasing p.d. increases currentB1
 current increases non-linearly so resistance increasesB1 [3]

[Total: 11]

CHEMISTRY ONLINE
 — TUITION —

- 3 (a) power = VI
current = $10.5 \times 103 / 230$
= 45.7 A
C1
M1
A0 [2]
- (b) p.d. across cable = 5.0 V
 $R = 5.0 / 46$
= 0.11 Ω
C1
C1
A1 [3]
- (ii) $R = \rho L / A$
 $0.11 = (1.8 \times 10^{-8} \times 16 \times 2) / A$
 $A = 5.3 \times 10^{-6} \text{ m}^2$
(wires in parallel, not series, allow max 1/3 marks)
C1
C1
A1 [3]
- (c) either power = V^2 / R or power $\propto V^2$
ratio = $(210 / 230)^2 = 0.83$
C1
A1 [2]
- (ii) resistance of cable is greater
greater power loss/fire hazard/insulation may melt
wire may melt/cable gets hot
M1
A1 [2]
- 4 (a) (i) $R = \rho L / A$
(ii) strain = $\Delta L / L$
either $\Delta R = \rho \Delta L / A$ or $R \propto L$ with ρ and A constant
dividing, $\Delta R / R = \Delta L / L$
B1
B1
B1
A0 [3]
- (b) Young modulus = stress / strain
strain = $72.0 / (1.20 \times 10^{-7} \times 2.10 \times 10^{11})$
= 2.86×10^{-3} (allow 1/350)
 $\Delta R = 2.86 \times 10^{-3} \times 4.17 = 1.19 \times 10^{-2} \Omega$
answer given to 3 sig. fig
C1
C1
A1
A1
B1 [5]

5	(a) (i)	resistance is ratio V/I (at a point)	B1	
		<i>either gradient increases or I increases more rapidly than V</i>	B1	[2]
		<i>(If states $R = \text{reciprocal of gradient}$, then 0/2 marks here)</i>		
	(ii)	current = 2.00 mA	C1	
		resistance = 2 000 Ω	A1	[2]
	(b) (i)	straight line from origin	M1	
		passing through (6.0 V, 4.0 mA) (allow $\frac{1}{2}$ square tolerance)	A1	[2]
	(ii)	individual currents are 0.75 mA and $\frac{1}{33}$ mA	C1	
		current in battery = 2.1 mA	A1	[2]
		<i>(allow argument in terms of $P = I^2 R$ or IV)</i>		
	(c)	same current in R and in C	M1	
		p.d. across C is larger than that across R	M1	
		so since power = VI , greater in C	A1	[3]
6	(a) (i)	$P = VI$ current = $60/240 = 0.25$ A	C1 A1	
	(ii)	$R (= V/I) = 240/0.25$ = 960 Ω	M1 A0	[3]
	(b)	$R = \rho L/A$ (wrong formula, 0/3) $960 = (7.9 \times 10^{-7} \times L)/(\pi \times \{6.0 \times 10^{-6}\}^2)$ $L = 0.137$ m <i>(use of $A = 2\pi r$, then allow 1/3 marks only for resistivity formula)</i>	C1 C1 A1	[3]
	(c)	e.g. the filament must be coiled/it is long for a lamp <i>(allow any sensible comment based on candidate's answer for L)</i>	B1	[1]
		Total		[7]

- 7 (a) (i) resistance = V/I C1
 = $6.0/(40 \times 10^{-3})$
 = 150Ω A1
 (no marks for use of gradient)
- (ii) at 8.0 V, resistance = $8.0/(50 \times 10^{-3}) = 160 \Omega$ C1
 change = 10Ω A1 [4]
- (b) (i) straight line through origin M1
 passes through $I = 40 \text{ mA}$, $V = 8.0 \text{ V}$ A1
- (ii) current in both must be 40 mA C1
 e.m.f. = $8.0 + 6.0 = 14.0 \text{ V}$ A1 [4]

