

# Sensing Devices

## Mark Scheme 1

<b>Level</b>	International A Level
<b>Subject</b>	Physics
<b>Exam Board</b>	CIE
<b>Topic</b>	Current of Electricity
<b>Sub Topic</b>	Sensing Devices
<b>Paper Type</b>	Theory
<b>Booklet</b>	Mark Scheme 1

**Time Allowed:** 66 minutes

**Score:** /55

**Percentage:** /100

CHEMISTRY ONLINE

A*	A	B	C	D	E	U
>85%	77.5%	70%	62.5%	57.5%	45%	<45%

1	(a)	$V/E = R/R_{\text{tot}}$ $1.0/1.5 = R/(R + 3900)$ $R = 7800\Omega$	or or or	$0.5 = I \times 3900$ $1.0 = 0.5R/3900$ $R = 7800\Omega$	C1 1 A0	[2]
	(b)	$V = 1.5 \times (7800/(7800 + 1250))$ $= 1.29 \text{ V}$	or or	$I = 1.5/(7800 + 1250)$ $V = IR = 1.29 \text{ V}$	C1 A1	[2]
	(c)	Combined resistance of R and voltmeter is 3900 $\Omega$ reading at 0 °C is 0.75 V			C1 A1	[2]
<b>Total</b>						[6]
2	(a)	$V_B = 1000 \text{ mV}$ when strained, $V_A = 2000 \times 121.5/(121.5 + 120.0)$ $= 1006.2 \text{ mV}$ change = 6.2 mV ( <i>allow 6 mV</i> )			A1	[3]
	(b)	1. resistor between $V_{\text{IN}}$ and $V^-$ <b>and</b> $V^+$ connected to earth resistor between $V^-$ and $V_{\text{OUT}}$			B1 B1	[2]
		2. P/+ sign shown on earth side of voltmeter			B1	[1]
	(ii)	ratio of $R_F/R_{\text{IN}} = 40$ $R_{\text{IN}}$ between 100 $\Omega$ and 10 k $\Omega$ ( <i>any values must link to the correct resistors on the diagram</i> )			M1 A1	[2]
3	(a)	(i) light-dependent resistor/LDR			B1	[1]
		(ii) strain gauge			B1	[1]
		(iii) quartz/piezo-electric crystal			B1	[1]
	(b)	resistance of thermistor decreases as temperature increses <i>etiher</i> $V_{\text{OUT}} = V \times R / (R + R_T)$ or current increases <u>and</u> $V_{\text{OUT}} = IR$ $V_{\text{OUT}}$ increases			M1 A1 A1	[3]
	(ii)	<i>either</i> change in $R_T$ with temperature is non-linear or $V_{\text{OUT}}$ is not proportional to $R_T$ / change in $V_{\text{OUT}}$ with $R_T$ is non-linear so change is non-linear			M1 A1	[2]

- 4 (a) 30 litres  $\rightarrow$  54 litres (*allow  $\pm 4$  litres on both limits*) B1 [1]
- (b) only 0.1 V change in reading for 10 litre consumption (*or similar numbers*) B1  
above about 60 litres gradient is small compared to the gradient at about 40 litres B1 [2]
- (ii) voltmeter reading (nearly) zero when fuel is left C1  
voltmeter reads only about 0.1 V when 10 litres of fuel left in tank A1 [2]  
(*"voltmeter reads zero when about 4 litres of fuel left in tank" scores 2 marks*)
- 5 (a) any value greater than, or equal to, 5 k $\Omega$  B1 [1]
- (b) (i) 'positive' shown in correct position B1 [1]
- (ii)  $V^+ = (500/2200) \times 4.5$   
 $\approx 1\text{ V}$   
 $V^- > V^+$  so output is negative  
green LED on, (red LED off)  
(*allow full ecf of incorrect value of  $V^+$* ) B  
M1  
A1 [3]
- (iii) *either  $V^+$  increases or  $V^+ > V^-$*   
green LED off, red LED on M1  
A1 [2]
- 6 (a) thin / fine metal wire B1  
lay-out shown as a grid B1  
encased in plastic B1 [3]
- (b) (i) gain (of amplifier) B1 [1]
- (ii) for  $V_{\text{OUT}} = 0$ , then  $V^+ = V^-$  or  $V_1 = V_2$  C1  
 $V_1 = (1000/1125) \times 4.5$  C1  
 $V_1 = 4.0\text{ V}$  A1 [3]
- (iii)  $V_2 = (1000 / 1128) \times 4.5$   
 $= 3.99\text{ V}$  C1  
 $V_{\text{OUT}} = 12 \times (3.99 - 4.00)$   
 $= (-) 0.12\text{ V}$  A1 [2]

- 7 (a) (i) strain gauge B1 [1]  
 (ii) piezo-electric / quartz crystal / transducer B1 [1]
- (b) circuit: coil of relay connected between sensing circuit output and earth B1  
 switch across terminals of external circuit B1  
 diode in series with coil with correct polarity for diode B1  
 second diode with correct polarity B1 [4]

- 8 (a) resistance of wire =  $\rho L / A$  ..... B1  
 as crack widens,  $L$  increases ..... M1  
 and  $A$  decreases ..... M1  
 so resistance increases ..... A0 [3]
- (b)  $\Delta L / L = \Delta R / R$  ..... B1  
 $= (146.2 - 143.0) / 143.0 \times 100$  ..... C1  
 $\Delta L / L = 2.24\%$  ..... A1 [3]

[Total: 6]

CHEMISTRY ONLINE  
 — TUITION —