

Electronics

Mark Scheme 4

Level	International A Level
Subject	Physics
Exam Board	CIE
Topic	Electronics
Sub Topic	
Paper Type	Theory
Booklet	Mark Scheme 4

Time Allowed: 63 minutes

Score: /52

Percentage: /100

CHEMISTRY ONLINE

A*	A	B	C	D	E	U
>85%	77.5%	70%	62.5%	57.5%	45%	<45%

- 1 (a) blocks labelled sensing device / sensor / transducer B1
processor / processing unit / signal conditioning B1 [2]
- (b) (i) two LEDs with opposite polarities (*ignore any series resistors*) M1
correctly identified as red and green A1 [2]
- (ii) correct polarity for diode to conduct identified M1
hence red LED conducts when input (+)ve or *vice versa* A0 [1]
- 2 (a) (i) - 9 V
- (ii) + 9 V (*both (i) and (ii) correct for the mark*) B1 [1]
- (b) \times \times B1
 \checkmark \times B1
 \checkmark \checkmark B1 [3]
 (no e.c.f. from (a))
- (c) (i) cct: thermistor and resistor in series M1
output connections across thermistor A1 [2]
- (ii) as temperature decreases, thermistor resistance increases B1
 p.d. across thermistor = $R_T / (R + R_T) \times V$ M1
 as R_T increases, output increases A1 [3]
- 3 (a) e.g. infinite (voltage) gain
 infinite input impedance
 zero output impedance
 infinite bandwidth
 infinite slew rate
 (*any three, 1 each*) B [3]
- (b) (i) negative (feedback) B1 [1]
- (ii) 1 gain (= $5.8/0.069$) = 84 B1 [1]
- (ii) 2 gain = $1 + 120/X$ C1
 $84 = 1 + 120/X$
 $X = 1.45 \text{ k}\Omega$ A1 [2]
- (iii) gain increases OR bandwidth reduced OR output increases B1 [1]

- 4 (a) $V_B = 1000 \text{ mV}$ C1
 when strained, $V_A = 2000 \times 121.5 / (121.5 + 120.0)$ M1
 $= 1006.2 \text{ mV}$ A1 [3]
 change = 6.2 mV (allow 6 mV)
- (b) (i) 1. resistor between V_{IN} and V^- and V^+ connected to earth B1
 resistor between V^- and V_{OUT} B1 [2]
2. P/+ sign shown on earth side of voltmeter B1 [1]
- (ii) ratio of $R_F / R_{IN} = 40$ M1
 R_{IN} between 100Ω and $10 \text{ k}\Omega$ A1 [2]
 (any values must link to the correct resistors on the diagram)
- 5 (a) any value greater than, or equal to, $5 \text{ k}\Omega$ B1 [1]
- (b) (i) 'positive' shown in correct position B1 [1]
- (ii) $V^+ = (500/2200) \times 4.5$
 $\approx 1 \text{ V}$ B1
 $V^- > V^+$ so output is negative M1
 green LED on, (red LED off) A1 [3]
 (allow full ecf of incorrect value of V^+)
- (iii) either V^+ increases or $V^+ > V^-$ M1
 green LED off, red LED on A1 [2]

CHEMISTRY ONLINE
 — TUITION —

- 6 (a) thin / fine metal wire
lay-out shown as a grid
encased in plastic
- B1
B1
B1 [3]
- (b) (i) gain (of amplifier)
- B1 [1]
- (ii) for $V_{OUT} = 0$, then $V^+ = V^-$ or $V_1 = V_2$
 $V_1 = (1000/1125) \times 4.5$
 $V_1 = 4.0\text{ V}$
- C1
C1
A1 [3]
- (iii) $V_2 = (1000 / 1128) \times 4.5$
 $= 3.99\text{ V}$
 $V_{OUT} = 12 \times (3.99 - 4.00)$
 $= (-) 0.12\text{ V}$
- C1
A1 [2]
- 7 (a) (i) strain gauge
- B1 [1]
- (ii) piezo-electric / quartz crystal / transducer
- B1 [1]
- (b) circuit: coil of relay connected between sensing circuit output and earth
switch across terminals of external circuit
diode in series with coil with correct polarity for diode
second diode with correct polarity
- B1
B1
B1
B1 [4]

CHEMISTRY ONLINE
— TUITION —